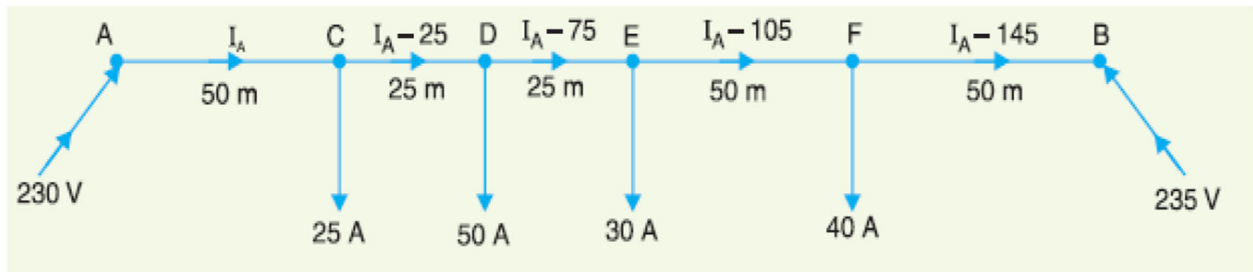



Name	Umar Hayyat
Roll No	2019-EE-360

Complex Engineering Problem(CEP) Session 2019 Fall 2021 Power Distribution System

Circuit:



Simulation:

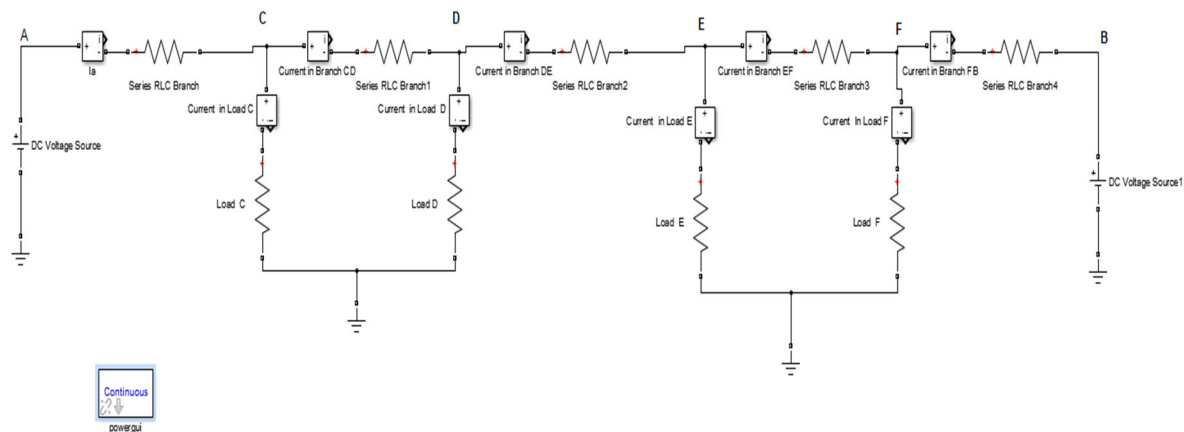

Results:

MEASUREMENTS :

1:	'I I _A	'	=	33.33 A
2:	'I Current in Branch FB'		=	-111.67 A
3:	'I Current in Branch EF'		=	-71.67 A
4:	'I Current in Branch DE'		=	-41.67 A
5:	'I Current in Branch CD'		=	8.33 A
6:	'I Current in Load E'		=	30.00 A
7:	'I Current in Load C'		=	25.00 A
8:	'I Current in Load D'		=	50.00 A
9:	'I Current In Load F'		=	40.00 A

Calculation:

Resistance of 2 wires of 1k m length = $2 * 0.3 = 0.6 \Omega$

Resistance of branch AC = $0.6 \left(\frac{50}{1000} \right) = 0.03 \Omega$

Resistance of branch CD = $0.6 \left(\frac{25}{1000} \right) = 0.015 \Omega$

Resistance of branch DE = $0.6 \left(\frac{25}{1000} \right) = 0.015 \Omega$

Resistance of branch EF = $0.6 \left(\frac{50}{1000} \right) = 0.03 \Omega$

Resistance of branch FB = $0.6 \left(\frac{50}{1000} \right) = 0.03 \Omega$

Voltage drops using Exact Method

$$V_B = V_A - (I_A R_{AC} + (I_A - 25) R_{CD} + (I_A - 75) R_{DE} + (I_A - 105) R_{EF} + (I_A - 145) R_{FB})$$

Put values of V_A , V_B , R_{AC} , R_{CD} , R_{DE} , R_{EF} and R_{FB} in Equ

$$235 = 230 - (0.03 I_A + 0.015 (I_A - 25) + 0.015 (I_A - 75) + 0.03 (I_A - 105) + 0.03 (I_A - 145))$$

$$235 = 230 - (0.12 I_A - 9)$$

$$I_A = \frac{239 - 235}{0.12} = 33.34$$

$$I_A = 33.34 \text{ A}$$

$$I_{AC} = I_A = 33.34 \text{ A}$$

$$I_{CD} = I_A - 25 = 33.34 - 25 = 8.34 \text{ A}$$

$$I_{DE} = I_A - 75 = 33.34 - 75 = -41.66 \text{ A}$$

$$I_{EF} = I_A - 105 = 33.34 - 105 = -71.66 \text{ A}$$

$$I_{FB} = I_A - 145 = 33.34 - 145 = -111.66 \text{ A}$$

$$\text{Voltage at point C} = V_C = V_A - I_A R_{AC} = 230 - (33.34 * 0.03) = 228.998$$

$$\text{Voltage at point D} = V_D = V_A - (I_{AC} R_{AC} + I_{CD} R_{CD})$$

$$V_D = 230 - (33.34 * 0.03 + 8.34 * 0.015)$$

$$V_D = 230 - 1.125$$

$$V_D = 228.875$$

$$\text{Voltage at point E} = V_E = V_B - (I_{BF} R_{FB} + I_{FE} R_{EF})$$

$$V_E = 235 - (111.66 * 0.03 + 71.66 * 0.03)$$

$$V_E = 229.5$$

$$\text{Voltage at point F} = V_F = V_B - I_{BF} R_{FB}$$

$$V_F = 235 - (111.66 * 0.03)$$

$$V_F = 231.65$$

$$\text{Voltage drop of C} = V_A - V_C = 230 - 228.998 = 1.002$$

$$\text{Voltage drop of D} = V_A - V_D = 230 - 228.875 = 1.125$$

$$\text{Voltage drop of E} = V_B - V_E = 235 - 229.5 = 5.5$$

$$\text{Voltage drop of F} = V_B - V_F = 235 - 231.65 = 3.35$$

Voltage drop by using approximate method

$$\text{Voltage drop } VD = IR$$

$$VD_C = 25 * 0.03$$

$$VD_C = 0.75V$$

$$VD_D = 50 * (0.03 + 0.015)$$

$$VD_D = 2.25V$$

$$VD_E = 30 * (0.03 + 0.03)$$

$$VD_E = 1.8V$$

$$VD_F = 40 * 0.03$$

$$VD_F = 1.2V$$

Total voltage drop b/w point A and B is:

$$\sum VD = VD_C + VD_D + VD_E + VD_F$$

$$\sum VD = 0.75 + 2.25 + 1.8 + 1.2$$

$$\sum VD = 3.15V$$

Comparision:

Currents	Simulation result	Calculated result
I _{AC}	33.33A	33.34A
I _{CD}	8.33A	8.34A
I _{DE}	-41.67A	-41.66A
I _{EF}	-71.67A	-71.66A
I _{FB}	-111.67A	-111.66A

The result of simulation are same as I calculated. The values that I calculate by using exact method are same as simulated. So, simulation use exact method.